

# *Digital System Design and Implementation*

## *Homework #1*

(Due by 03/11 PM 8:00)

**Note:** Please **upload your codes** and **hand in the hardcopy** of this experiment including

- Verilog Codes (60%)
- Test bench (20%)
- Input/Output waveforms.(20%)

For even-numbered students, please implement Fig. 1. For odd-numbered students, please implement Fig. 2. The logic gates of the respective sub-block are described in Fig. 3.

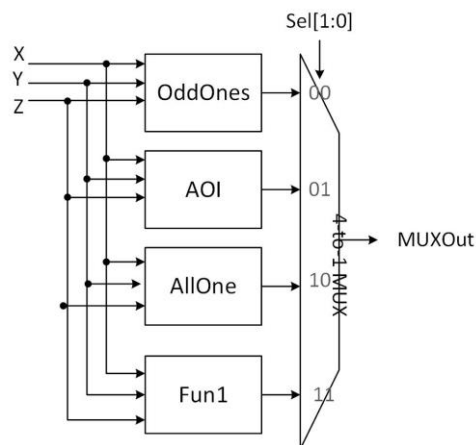


Fig. 1 Block diagram of type 1

 


Fig. 2 Block diagram type 2

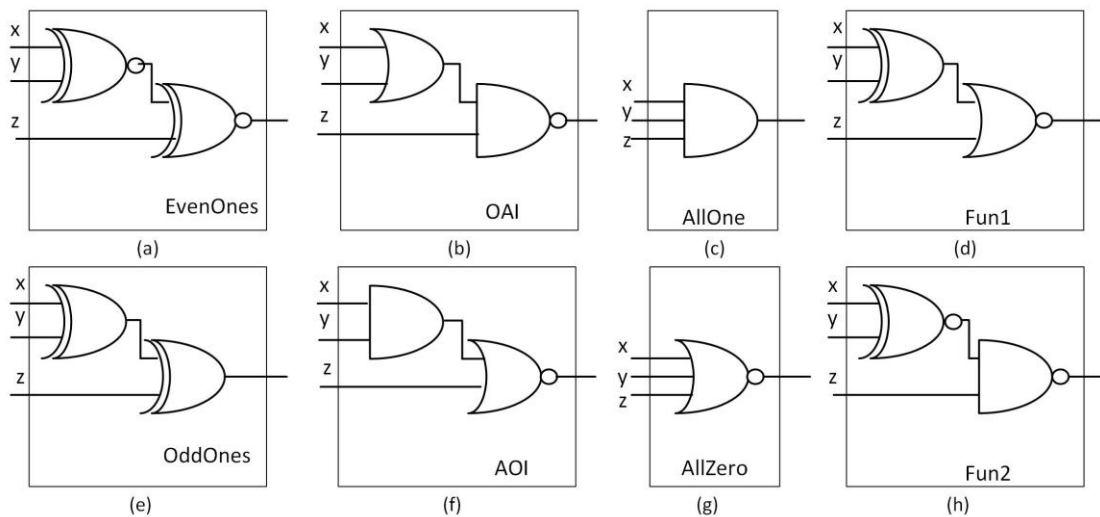


Fig. 3 Logic gates of each sub-block.

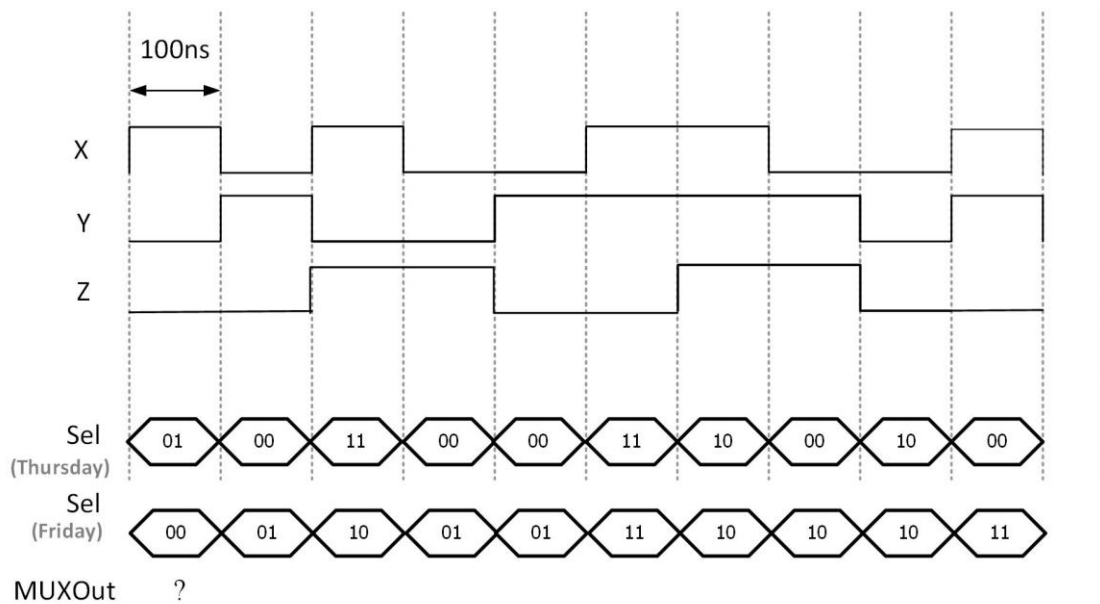


Fig. 4 Test pattern.

- For even-numbered students,
  - Please use Verilog to describe the digital circuits in Fig. 1.
  - Write a test bench to test your design.
  - The input waveforms are given in Fig. 4. Note the difference for signal “Sel[1:0]” of students with lab. time on Thursday and Friday.
- For odd-numbered students,
  - Please use Verilog to describe the digital circuits in Fig. 2.
  - Write a test bench to test your design.
  - The input waveforms are given in Fig. 4. Note the difference for signal “Sel[1:0]” of students with lab. time on Thursday and Friday.